

1. Diode Characteristics (LED, Silicon, Zener)

Objective:

To plot the I-V characteristics for different diodes: LED, Silicon, and Zener.

- **LED & Silicon: Only forward bias.**
- **Zener Diode: Both forward and reverse bias.**

Summary:

- **Forward bias: Diode conducts after threshold (cut-in) voltage.**
- **Reverse bias: No conduction until Zener breakdown (Zener diode only).**
- **Zener effect: Sharp reverse conduction at breakdown voltage (voltage regulation).**
- **LED: Emits light when forward biased due to photon emission.**

Viva Questions:

Easy:

- **What is the threshold voltage of a silicon diode?**
→ ~0.7V
- **What is the threshold voltage of an LED?**
→ ~1.8V to 3.3V depending on color.
- **What is a Zener diode used for?**
→ Voltage regulation in reverse bias.

Medium:

- **Why doesn't a normal diode conduct in reverse bias?**
→ Depletion region widens and blocks current flow.
- **How is Zener breakdown different from Avalanche breakdown?**
→ Zener: quantum tunneling; Avalanche: carrier multiplication.

Hard:

- Explain how doping affects breakdown voltage in Zener diodes.
→ Heavily doped → narrow depletion → low breakdown voltage.
 - Why does an LED emit light but silicon diode doesn't?
→ LED is made from direct bandgap materials; silicon is indirect.
-

2. Half-Wave & Full-Wave Rectifiers

 **Objective:**

To demonstrate the conversion of AC to DC using diode-based rectifiers.

 **Summary:**

- Half-Wave Rectifier: Passes one half of AC cycle using a single diode.
- Full-Wave Rectifier: Uses both halves (center-tap or bridge).
- Output: Pulsating DC (filtered optionally).
- Application: Power supplies.

 **Viva Questions:**

Easy:

- What is a rectifier?
→ Circuit that converts AC to DC.
- What is the purpose of a filter capacitor in rectifiers?
→ Smoothens ripples in output voltage.

Medium:

- Why is full-wave rectification preferred over half-wave?
→ Higher efficiency, smoother output.
- What is the ripple frequency of a full-wave rectifier?
→ Twice the input AC frequency.

Hard:

- Derive the expression of ripple factor for half and full-wave rectifiers.
 - What is PIV (Peak Inverse Voltage)?
→ Maximum reverse voltage a diode must withstand.
-

3. Transistor DC Analysis (Voltage Divider Bias)

 **Objective:**

To obtain input and output characteristics of a BJT using voltage divider bias.

 **Summary:**

- Voltage Divider Bias: Resistors bias base voltage for stability.
- Input Graph: I_B vs V_{BE} (base-emitter).
- Output Graph: I_C vs V_{CE} (collector-emitter).
- Establishes Q-point (operating point).

 **Viva Questions:**

Easy:

- What are the terminals of a BJT?
→ Base, Collector, Emitter.
- What is β (beta) of a transistor?
→ Ratio of collector current to base current (I_C/I_B).

Medium:

- Why use voltage divider bias instead of fixed bias?
→ Better thermal stability.
- What is the typical V_{BE} for a silicon transistor?
→ $\sim 0.7V$

Hard:

- Explain how the Q-point can shift due to temperature.
→ I_C increases → V_{CE} decreases → possible saturation.

- Derive the expression for base bias voltage in voltage divider configuration.
-

4. Transistor AC Analysis (Voltage Divider Bias)

Objective:

To observe amplification behavior of a transistor under AC input.

Summary:

- Uses small signal AC on top of DC bias.
- Coupling capacitors block DC, pass AC.
- Measures voltage gain (A_v) = V_{out} / V_{in} .
- BJT operates in active region for amplification.

Viva Questions:

Easy:

- Why do we need coupling capacitors?
→ To prevent DC bias disturbance between stages.

Medium:

- What causes phase reversal in transistor amplifiers?
→ In common-emitter, output is 180° out of phase with input.

Hard:

- Explain bandwidth and its importance in amplifiers.
→ Range of frequencies amplifier can handle efficiently.
 - Why does gain drop at high frequencies?
→ Internal capacitances and parasitic effects.
-

5. 2-bit Comparator using LM324

Objective:

To compare two 2-bit binary numbers and generate logical output signals ($A > B$, $A < B$, $A = B$).

Summary:

- Uses LM324 quad op-amp IC.
- Inputs converted to analog voltages (if necessary).
- Comparators output HIGH or LOW depending on voltage difference.
- Implements basic digital logic using analog components.

Viva Questions:

Easy:

- What is the function of a comparator?
→ Outputs HIGH or LOW based on comparison between two inputs.

Medium:

- Why choose LM324 for comparator circuits?
→ Has 4 op-amps, works on single supply, low cost.

Hard:

- How to convert a 2-bit binary input into analog for comparison?
→ Use weighted resistors or DAC logic.
- Can we use a comparator to build ADC? How?
→ Yes, using multiple comparators (flash ADC architecture).

6. 3-bit Parallel ADC using LM324 and 74LS148N

Objective:

To convert an analog voltage into 3-bit digital output using comparators and a priority encoder.

Summary:

- LM324 compares input with reference voltages.
- Each comparator gives a HIGH/LOW depending on comparison.
- 74LS148N encodes which comparator was last HIGH → outputs 3-bit binary code.
- Very fast conversion → called Flash ADC.

Viva Questions:

Easy:

- What does ADC stand for?
→ Analog to Digital Converter.

Medium:

- How does a flash ADC work?
→ Multiple comparators compare input with known references simultaneously.

Hard:

- Why use 74LS148N?
→ 8-to-3 line priority encoder simplifies output logic.
- What is quantization error in ADC?
→ Error due to representing continuous input as discrete levels.

General Viva Tips:

- Revise circuit diagrams for each experiment.
- Understand input/output behavior clearly.
- Practice drawing graphs (diode I-V, transistor input/output).
- Be familiar with IC pinouts: LM324, 74LS148N.
- Know basic formulae: gain, ripple factor, bias voltages.
- Be ready to explain real-life applications of each circuit.